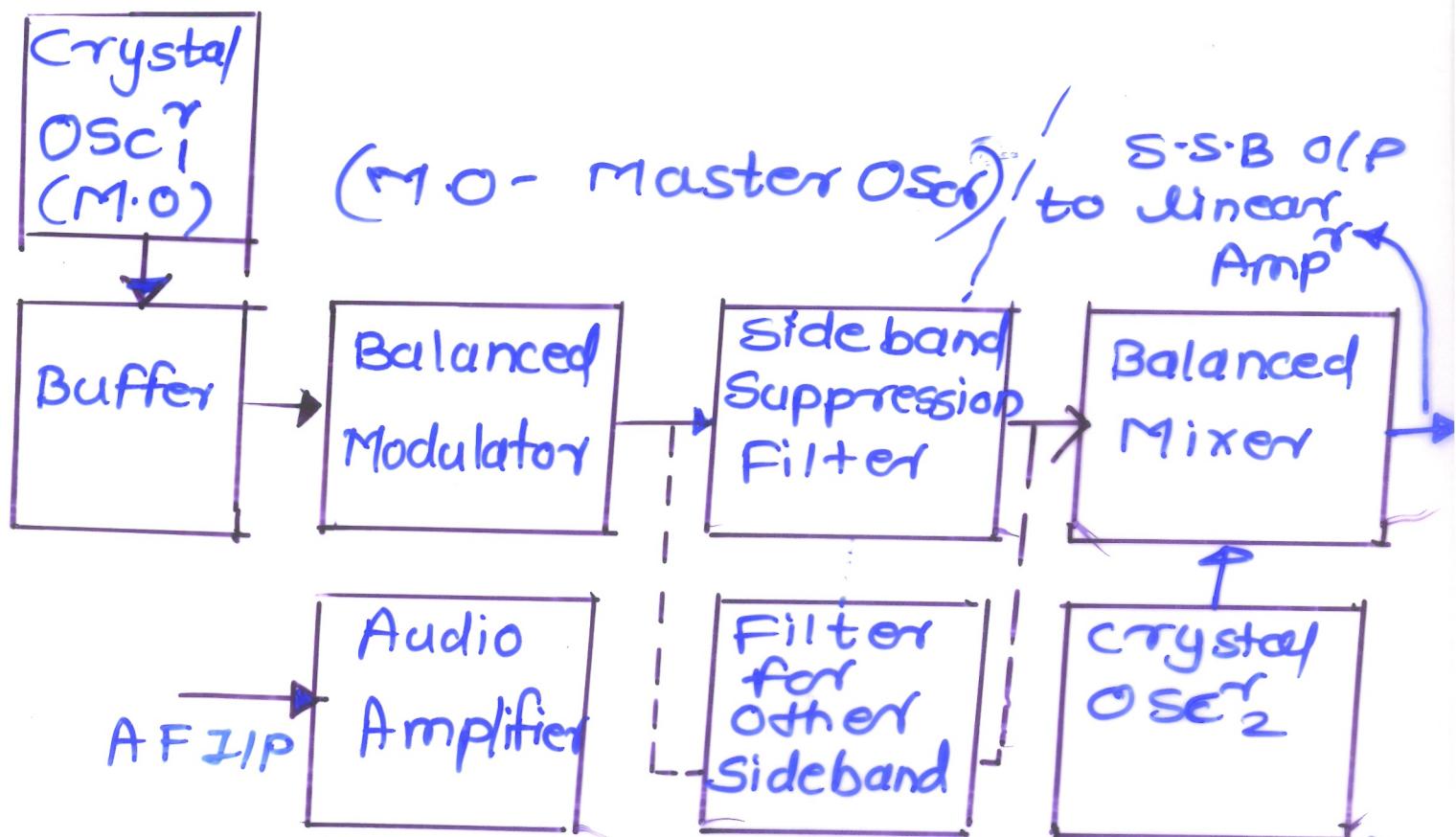


# FILTER METHOD

(3)



Crystal Osc<sup>r</sup>1 → Generates carrier freq

Buffer → Provides isolation b/w M.O and rest of the cct.

It has high IIP Impedance & low O/P Impedance.


Avoids loading effect

- Balanced Modulator gives DSBSC signal.
- One of the sideband is selected by means of sideband suppression filter.

- Filter must have a flat passband and extremely high attenuation outside the passband.

$$\text{Q}_S = \frac{f_m}{\text{B.W.}}, \quad f_m = 50 \text{ Hz}, Q_S \text{ is very high}$$

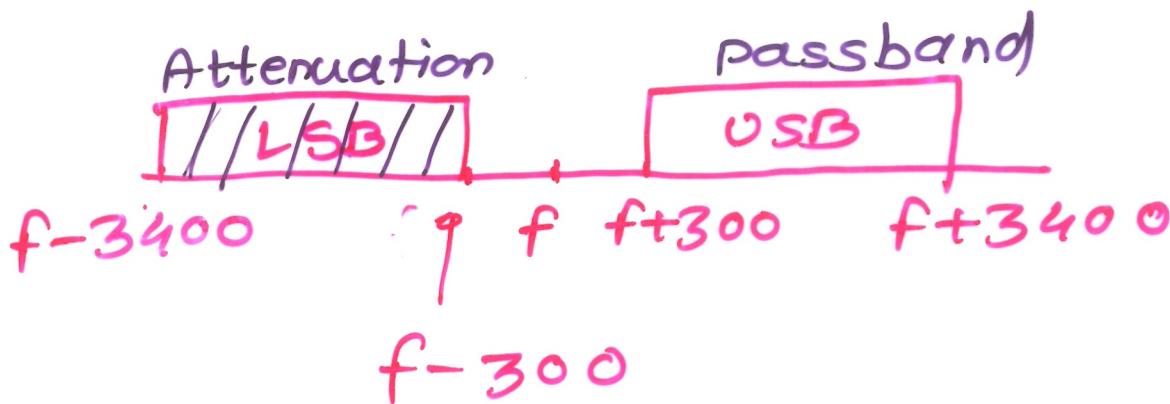- for lower modulating freq 300Hz  
 $f+300$  (USB),  $f-300$  (LSB)  
 and higher modulating freq  
 $f+3400$  (USB),  $f-3400$  Hz



- Filter response must change from full attenuation to zero attenuation over a range of 600Hz

- Types of filter  
 LC, crystal, ceramic, mechanical filter
- LC filter can not be used above 100 kHz as attenuation outside passband is insufficient.

- Crystal or ceramic filters are better only above 1MHz upto 20 MHz.
- Mechanical filters are  
small size  
good passband and attenuation characteristics.  
Adequate upper freq limit (500kHz)  
Hence used for S.S.B
- Frequency Upconversion  
Maximum operating freq is much below usual transmitting frequency so balanced Mixer is used for freq upconversion.  
( $\text{O}_8$ , filter cht)
- O/P Balanced mixer is given to linear amplifiers (class B or A) so as to avoid distortion

## Advantages

(II)

- ① Adequate sideband suppression (50 dB)
- ② Sideband filter also helps to attenuate the carrier, adding safety feature which is absent from other two methods.
- ③ Bandwidth is sufficiently flat and wide.
- ④ Simpler as compared to other two methods.


## Disadvantages

- ① Frequency upconversion is needed.
- ② Very low audio frequencies can not be transmitted (below 50 Hz) (very large Q is required not practically)
- ③ Expensive filters are required one for each sideband
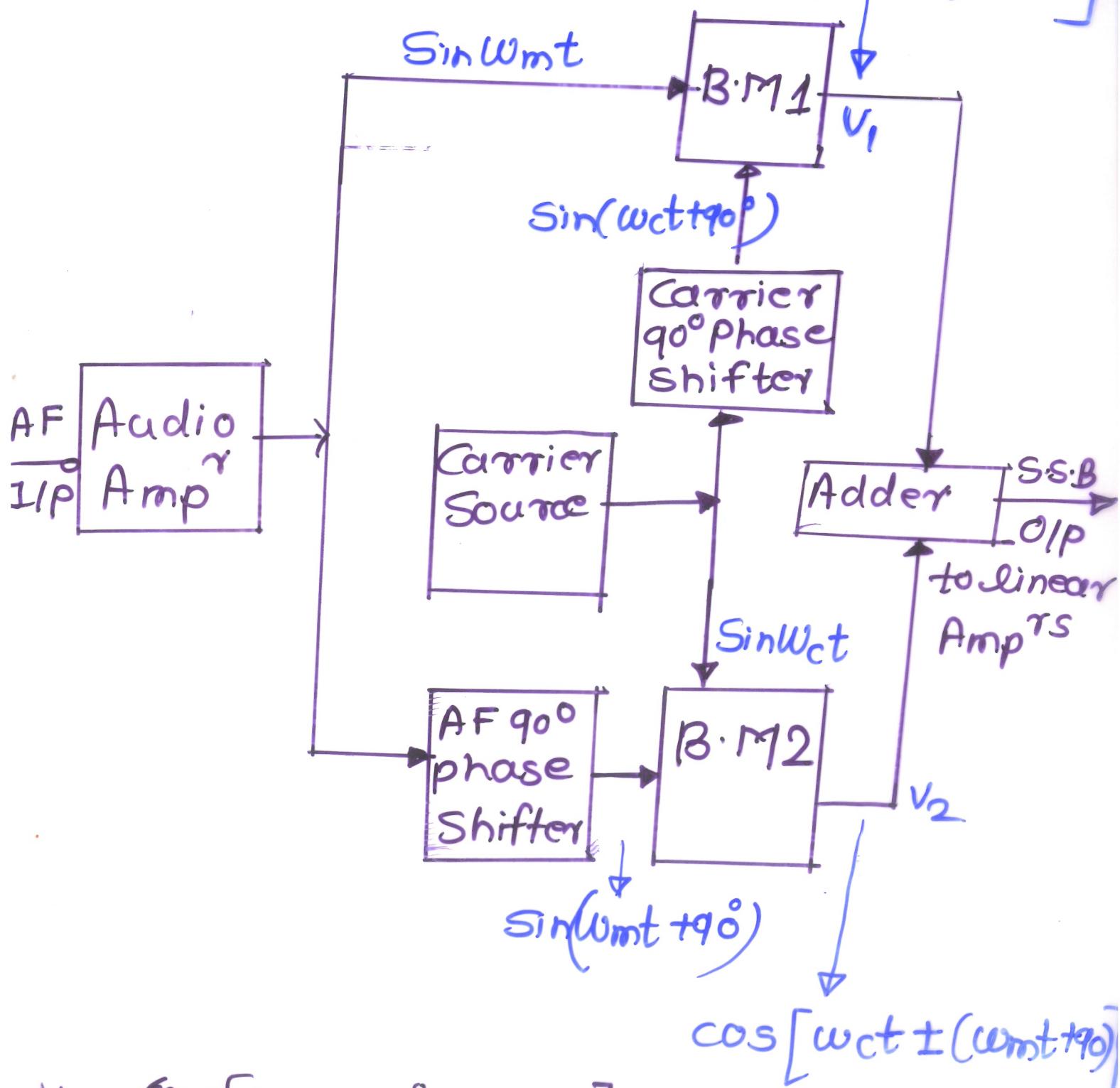
# Phase Shift Method

12

$$\cos[(\omega_c t + 90^\circ) \pm \omega_m t]$$



$$V_1 = \cos[(\omega_{ct} + 90^\circ) - \omega_{mt}] - \cos[\omega_{ct} + 90^\circ + \omega_{mt}]$$

$$= \cos(\omega_{ct} - \omega_{mt} + 90^\circ) - \cos[\omega_{ct} + \omega_{mt} + 90^\circ]$$

$$V_2 = \cos[\omega_{ct} - (\omega_{mt} + 90^\circ)] - \cos[\omega_{ct} + (\omega_{mt} + 90^\circ)]$$

$$= \cos[\omega_{ct} - \omega_{mt} - 90^\circ] - \cos[\omega_{ct} + \omega_{mt} + 90^\circ]$$

$$V_O = V_1 + V_2$$

(13)

$$\vec{v} = 2 \cos[\omega_{ct} + \omega_{mt} + 90^\circ] \quad \text{USB.}$$

For LSB Generation

① carrier phase shift - 90°

$$V_1 = \cos[\omega_{ct} - 90^\circ - \omega_{mt}] - \cos[\omega_{ct} - 90^\circ + \omega_{mt}]$$

$$V_2 = \cos[\omega_{ct} - \omega_{mt} - 90^\circ] - \cos[\omega_{ct} + \omega_{mt} + 90^\circ]$$

$$V_O = V_1 + V_2 = 2 \cos[\omega_{ct} - \omega_{mt} - 90^\circ]$$

② Interchange position of carrier source and carrier 90° phase shifter.

$$V_1 = \cos(\omega_{ct} + 90^\circ - \omega_{mt}) - \cos(\omega_{ct} + \omega_{mt} + 90^\circ)$$

$$V_2 = \cos[\omega_{ct} - \omega_{mt}] - \cos[\omega_{ct} + \omega_{mt}]$$

$$V_O = V_1 + V_2 = 2 \cos[\omega_{ct} - \omega_{mt} + 90^\circ] - \cos[\omega_{ct} + 90^\circ + \omega_{mt} + 90^\circ]$$

$$V_O = V_1 + V_2 = 2 \cos[\omega_{ct} - \omega_{mt}] - 90^\circ \text{ phase shift to Audio Signal}$$

$$V_1 = \cos[\omega_{ct} - \omega_{mt} + 90^\circ] - \cos[\omega_{ct} + \omega_{mt} + 90^\circ]$$

$$V_2 = \cos[\omega_{ct} - \omega_{mt} + 90^\circ] - \cos[\omega_{ct} + \omega_{mt} - 90^\circ]$$

$$V_o = 2 \cos[\omega_c t - \omega_m t + 90^\circ]$$

(14)

## Advantages →

- ① frequency upconversion is not needed.
- ② Lower audio frequencies can be transmitted.
- ③ It is easy to switch from one sideband to other sideband.


## Disadvantages →

- ① Exact  $90^\circ$  phase shift is required otherwise unwanted sideband will not be removed completely.
- ② Attenuation for unwanted sideband should be at least 40 dB.  
so phase shift should be less than  $1^\circ$
- ③ 2 Balanced Modulators must give exactly same output.  
(This assumption was made in proof) otherwise cancellation

Design of  $90^\circ$  phase shifting N/W for the modulating signal is extremely critical. 15


because of these reasons it is not used commercially. But used widely by amateurs, since it tends to be rather expensive.

### Third Method

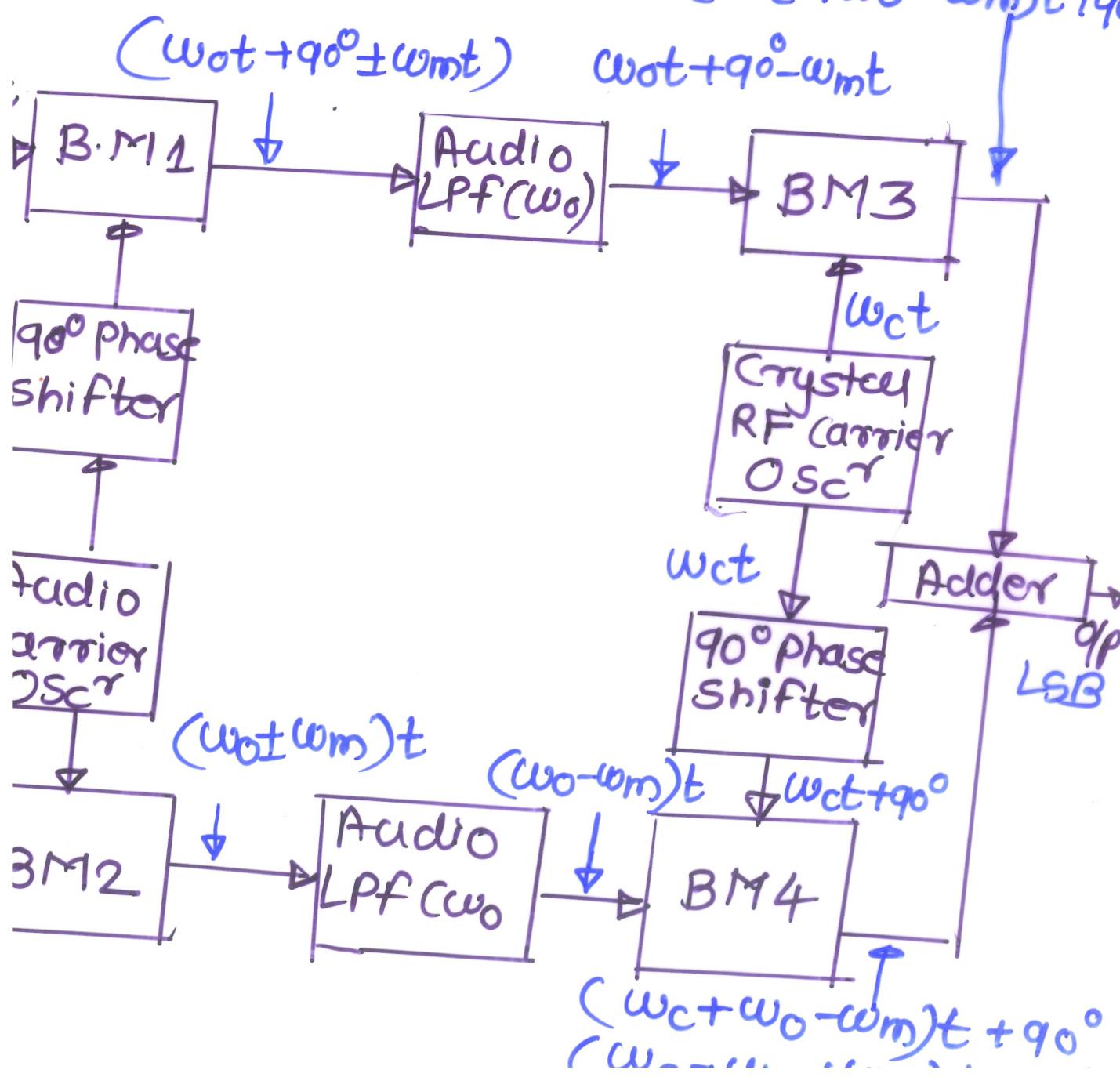

Design of  $90^\circ$  phase shifting N/W or the modulating signal is extremely critical. 15  
 because of these reasons it is not used commercially. But used widely by amateurs, since filter tends to be rather expensive.

### Third Method

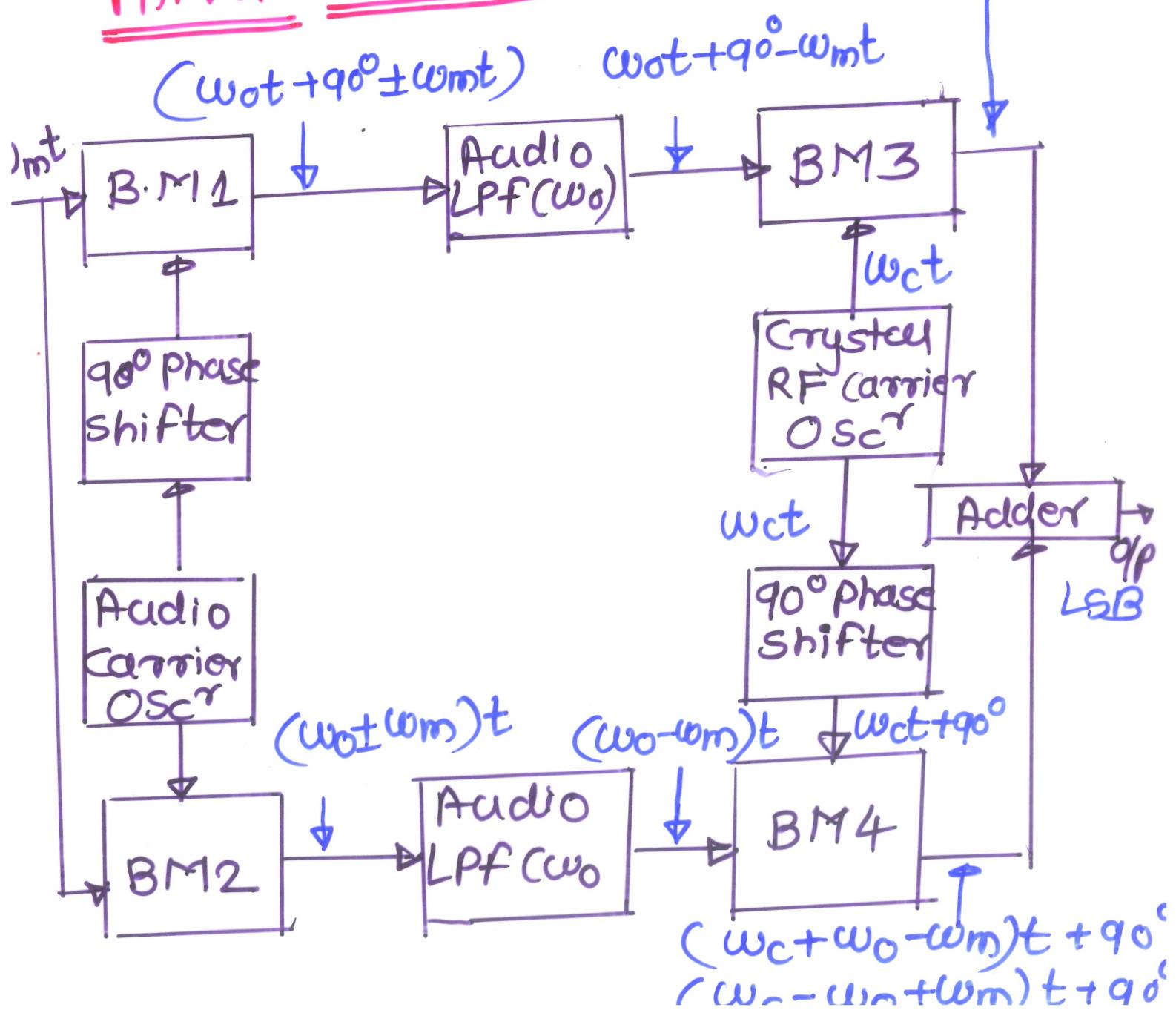

Phase shift is not given to whole range of audio band. (16)

Audio signal is first modulated onto an audio subcarrier  $f_o$ . This audio subcarrier is in the middle of audio band say 1650Hz. Phase shift is first applied to this frequency only.

O/p of B.M 1 + B.M 2 contains USB & LSB both shifted in phase by  $90^\circ$  and LSB & USB respectively.

Lower sidebands are selected and given as I/P to B.M 3 + B.M 4

O/P of B.M 3 and B.M 4 are as follows  
B.M 3  $\rightarrow f_c + f_o - f_m + 90^\circ$

$f_c - f_o + f_m - 90^\circ \times$

B.M 4  $\rightarrow f_c + f_o - f_m + 90^\circ$

$f_c - f_o + f_m + 90^\circ \times$

Added O/P is LSB with  $f_c + f_o - f_m + 90^\circ$  having carrier freq  $f_c + f_o$  and phase shift of  $90^\circ$ . USB and other sideband removed.

(17)

## USB Generation

Interchange carrier I/P to BM3 + BM4

oFBM3 is

$$ct + q_0 - w_{ot} - q_0 + w_{mt}) +$$

$$\omega ct + q_0 + w_{ot} + q_0 - w_{mt}) \times$$

P BM4 is

$$(ct - w_{ot} + w_{mt}) + (\omega ct + w_{ot} - w_{mt}) \times$$

At adder o/p we get USB with  
freq  $f_c - f_o + f_m + \dots$

we get upper sideband with carrier  
freq  $f_c - f_o$

### Advantages of Third method

① Adequate attenuation (50dB) for  
~~unwanted sideband~~

②

## Advantages of Third Method

(18)

- ① Does not require sideband suppression filter nor a wideband audio phase shift
- ② Low audio frequencies can be transmitted
- ③ No need for frequency up conversion.
- ④ Easy to switch from one sideband to other sideband.

## Disadvantages of Third Method

- ① Whistle will exist at that frequency if the balance of the low frequency balanced modulator deteriorates
- ② Most complex.
- ③ 4 BM are used where we assumed perfect o/p

Filter Method works well for present requirement.