
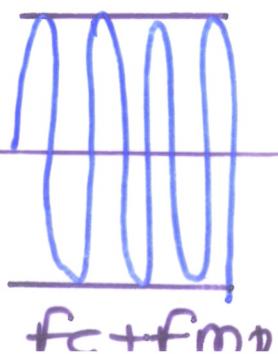
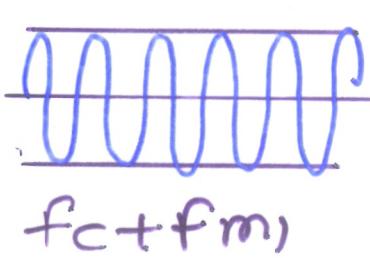
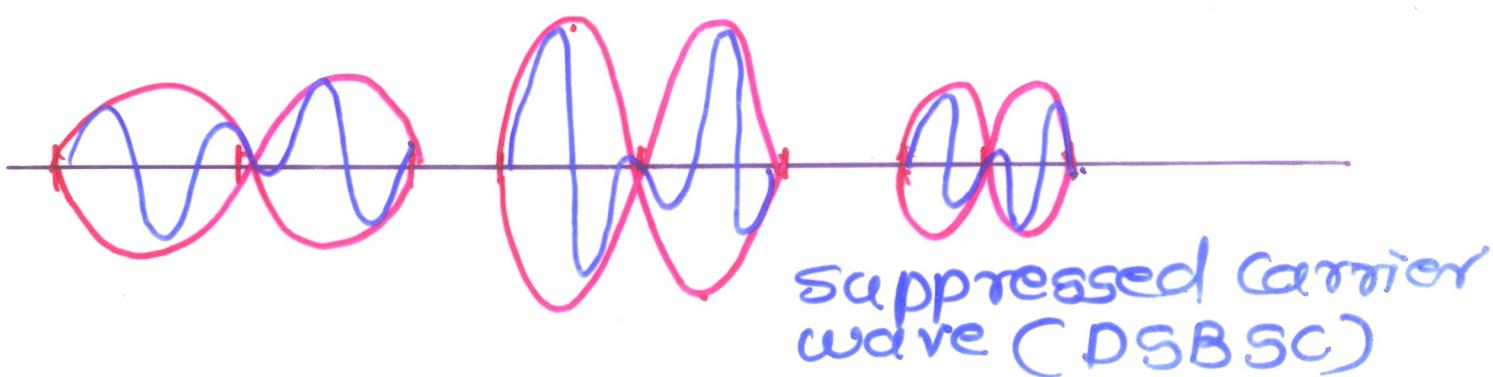
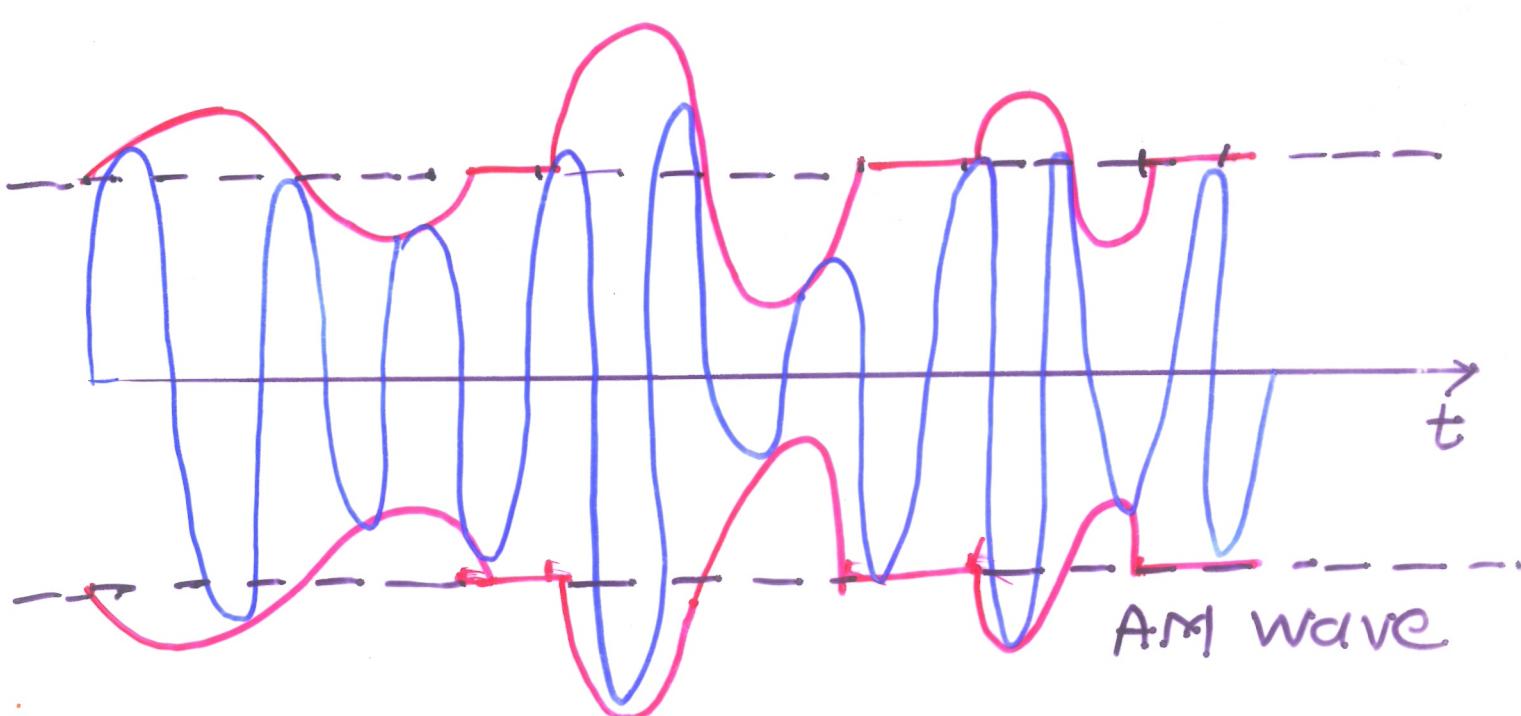


Single Sideband Techniques

10

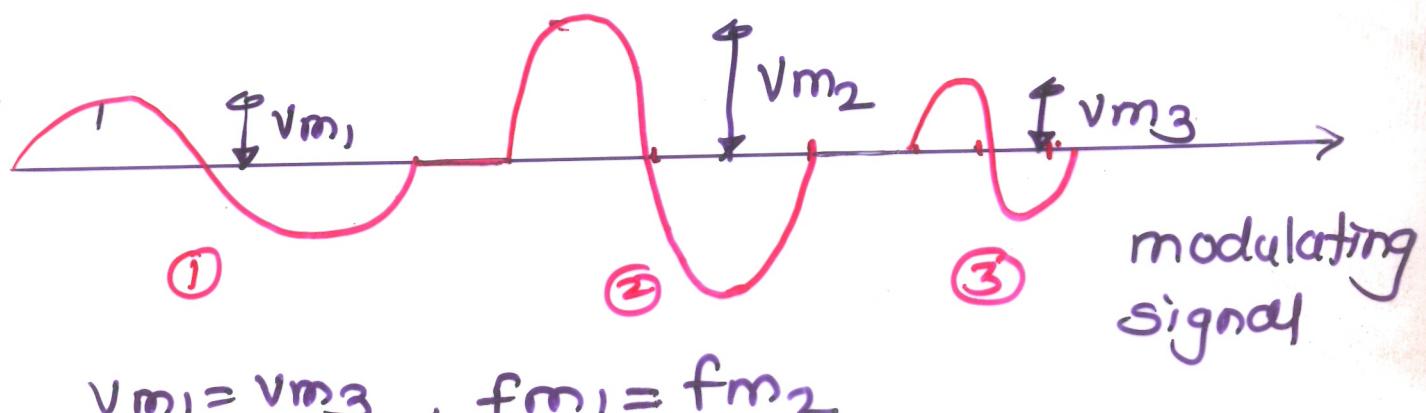

Advantages of S.S.B over DSBFC

18


- ① Less B.W requirement $BW = fm$
This allows more signals to be transmitted in the same freq range
- ② power saving 83-33% for $m=1$
- ③ Reduction in interference due to noise
 BW reduces so noise also reduces

Disadvantages

- ④ Generation & reception of S.S.B signal is complicated.
- ⑤ S.S.B T_x^* & R_x^* need to have excellent freq stability
A slight change in frequency will hamper the quality of transmitted & received signal. Therefore S.S.B is not generally used for transmission of good quality of music. It is used for speech communication

frequency spectrum

(2)

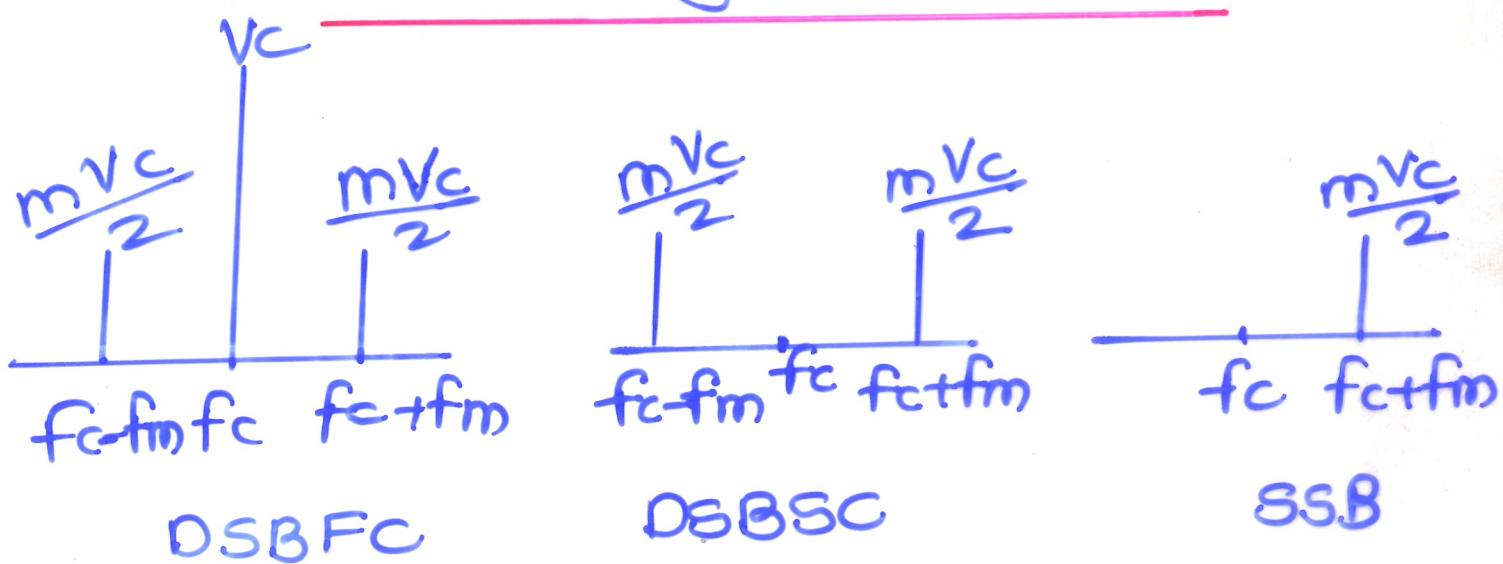

Effect of Nonlinear Resistance

Relationship b/n voltage & current in a linear resistance is given by

$$i = bV \rightarrow (1)$$

$b \rightarrow$ constant of proportionality
for Resistor b is called transconductance


If we apply the eqⁿ to nonlinear resistance

$$i = a + bV + cV^2 + dV^3 + \text{higher powers of } V \rightarrow (2)$$

where $a \rightarrow$ dc component

$b \rightarrow$ transconductance

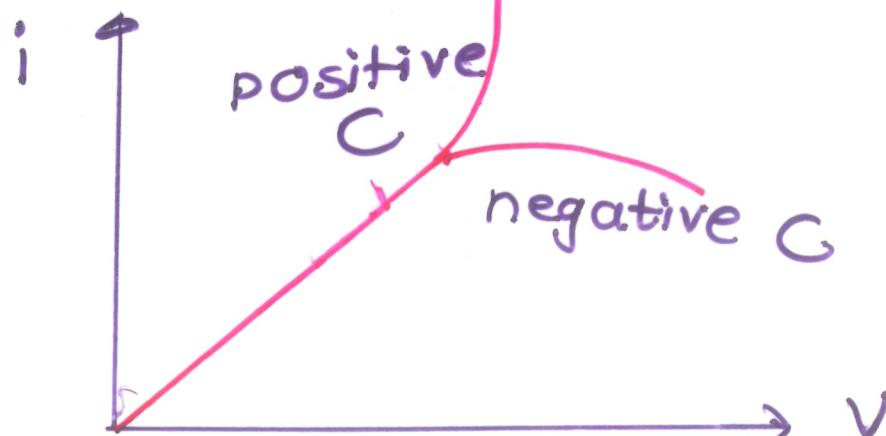$c \rightarrow$ coefficient of nonlinearity



Two input voltages V_1 and V_2 are applied simultaneously to the gate of FET

$$\text{Let } V_1 = V_c \sin \omega_c t \rightarrow \textcircled{3}$$

$$V_2 = V_m \sin \omega_m t \rightarrow \textcircled{4}$$

$$i = a + bV + cV^2 \rightarrow \textcircled{5}$$

$$i = a + b(V_c \sin \omega_c t + V_m \sin \omega_m t) + c(V_c \sin \omega_c t + V_m \sin \omega_m t)^2 \rightarrow \textcircled{6}$$

$$= a + bV_c \sin \omega_c t + bV_m \sin \omega_m t + cV_c^2 \sin^2 \omega_c t + cV_m^2 \sin^2 \omega_m t + 2cV_c \sin \omega_c t \cdot V_m \sin \omega_m t$$

$$= a + bV_c \sin \omega_c t + bV_m \sin \omega_m t + \frac{cV_c^2}{2}(1 - \cos 2\omega_c t) + \frac{cV_m^2}{2}(1 - \cos 2\omega_m t) + \frac{2cV_c V_m}{2} [\cos(\omega_c - \omega_m)t - \cos(\omega_c + \omega_m)t]$$

$$= \left(a + \frac{1}{2}cV_c^2 + \frac{1}{2}cV_m^2 \right) + bV_c \sin \omega_c t + bV_m \sin \omega_m t - \left[\frac{1}{2}cV_c^2 \cos 2\omega_c t + \frac{1}{2}cV_m^2 \times \cos 2\omega_m t \right] + cV_c V_m \cos(\omega_c - \omega_m)t - cV_c V_m \cos(\omega_c + \omega_m)t \rightarrow \textcircled{7}$$


1st term is the dc component. [4]
Second term is the carrier component
Third term is the modulating signal
Fourth term consists of harmonics
of the carrier and modulating signal
) Fifth term represents the
lower side band voltage
) Sixth term represents the
upper sideband voltage.

Eqⁿ ⑥ shows that when two frequencies
are passed through a non-linear
resistance, the process of amplitude
modulation takes place.

In Practical modulation cct, the
voltage would be developed across
a cct tuned to the carrier freq.
Bandwidth is large enough to
pass two sideband frequencies but
no others.

Balanced Modulator

(5)

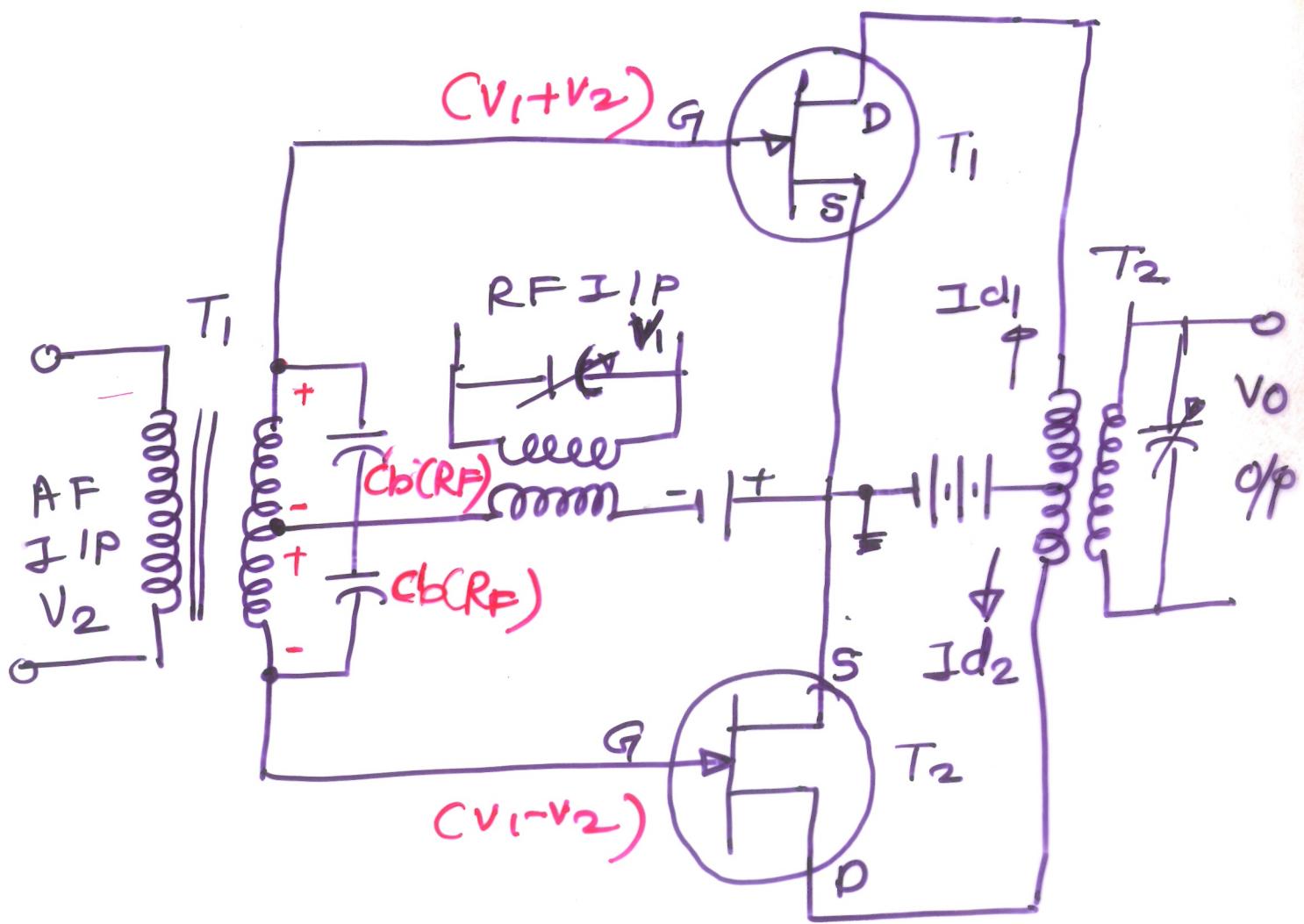

modulating voltage V_2 is fed in push-pull.

carrier voltage V_1 is fed in parallel to a pair of identical diodes or FETs.

I/P voltage is $V_1 + V_2$ at gate of FET $_1$ (T_1) and $V_1 - V_2$ at gate of FET $_2$ (T_2)

Assume perfect symmetry ⑥

Then proportionality constants will be same for both FGTs

$$Id_1 = \alpha + b(v_1 + v_2) + c(v_1 + v_2)^2 \rightarrow ①$$

$$Id_2 = \alpha + b(v_1 - v_2) + c(v_1 - v_2)^2 \rightarrow ②$$

$$i = Id_1 - Id_2 \rightarrow ③$$

$$= 2bV_2 + 4cV_1V_2 \rightarrow ④$$

In absence of modulating signal drain currents are equal in magnitude but opposite in direction so induces zero secondary voltage.

∴ carrier gets suppressed.

$$\text{Replace } v_1 = V_c \sin \omega_c t \quad] \rightarrow ⑤$$

$$v_2 = V_m \sin \omega_m t$$

$$i = 2bV_m \sin \omega_m t + 4c V_c V_m \sin \omega_c t \sin \omega_m t$$
$$= 2bV_m \sin \omega_m t + 2c V_c V_m [\cos(\omega_c - \omega_m)t - \cos(\omega_c + \omega_m)t]$$

O/P voltage $v_o = \propto i$

$$v_o = 2\alpha bV_m \sin \omega_m t + 2\alpha c V_c V_m \times [\cos(\omega_c - \omega_m)t - \cos(\omega_c + \omega_m)t] \rightarrow ⑦$$

Let $P = 2B\omega V_m$, $Q = 2\omega C V_c V_m$ ⑦

+ modulating signal

$$V_o = P \sin(\omega_m t) + Q \cos(\omega_c - \omega_m)t \rightarrow LSB$$

$$- Q \cos(\omega_c + \omega_m)t \rightarrow USB \quad \text{⑧}$$

Tuning of o/p amplifier will remove modulating signal. Only two side-bands will be present in o/p.